



SIMPLE CPU DESIGN: VERILOG LAB 4

APPROACH

- 1) The CPU has two components Control Unit (CU) and ALU (Arithmetic and Logical Unit)
- 2) **Control Unit:**
 - a) It generates the one-hot output (8-bit) from the 3 MSBs and passes it to ALU using 3x8 decoder.
 - b) It separates the two operands (bits [15:8] and [7:0]) and passes it to ALU.
- 3) **Arithmetic and Logical Unit**
 - a) It has 8 modules (and necessary submodules for them) for the 8 operations.
 - b) The input operands are fed into all the module circuits.
 - c) The correct output is selected using the one-hot input from CU (by ANDing respective bit with the output of each module).
 - d) There is an additional flag bit which gets set whenever there is a carry or borrow.

DIAGRAM

INSTRUCTION

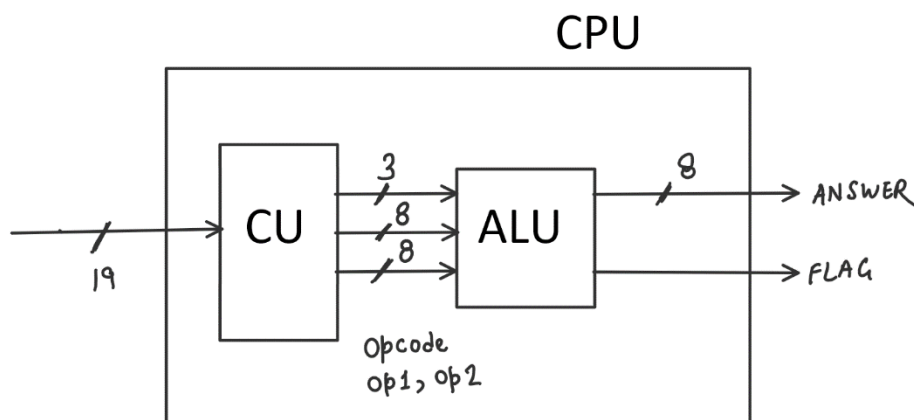 

MODULES

1) Control Unit

a) 3x8 Decoder

- It creates 8-bit one-hot output using the 3 input bits by generating all the minterms.

2) Arithmetic and Logical Unit

a) XOR bitwise

- Both operands were XORed using an 8-bit array of XOR gates.

b) ADDITION

- The 8-bit adder was made using 8 full adder modules (Ripple Carry Adder).
- Each full adder module had 2 half adder modules along with an OR gate

c) SUBTRACTION

- Subtraction was performed by adding the 2's complement of second operand to the first.
- This required an 8-bit adder module instantiation from the previous part.

d) AND bitwise

- Both operands were ANDed using an 8-bit array of AND gates.

e) OR bitwise

- Both operands were ORed using an 8-bit array of OR gates.

f) NOT bitwise

- First operand is NOTed using an 8-bit array of NOT gates.

g) INCREMENT

- **Optimisation:** Instead of instantiating a full 8-bit adder module, I created an incrementer using only 8 half adders.

h) DECREMENT

- **Optimisation:** Instead of instantiating a full 8-bit adder module, I created a decrementer using only 8 half adders.

i) SELECTING THE CORRECT OUTPUT

- Each output is ANDed with the decoder input to get the required answer.

OUTPUT

- Final Output

